

Report on Event 4 of Lab Component

CMOS VLSI Circuits (EC630)

Covering the course objective

CO 4: Design, Demonstrate and validate the analog and digital CMOS circuits using Cadence tool / Electric tool, document and give an effective presentation.

Title: Part – B Analog Circuits

Name: Mohamed Farhan Fazal

Roll No: 27

USN: 01JST18EC055

Division: A

Submitted to

Prof. Halesh M. R
Assistant Professor, Dept. of ECE

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING
2021

TABLE OF CONTENT


TABLE OF CONTENT	2
COMMON SOURCE AMPLIFIER	4
SCHEMATIC	4
SCHEMATIC RESULT ANALYSIS	4
DC ANALYSIS	4
TRANSIENT ANALYSIS	5
AC ANALYSIS	5
LAYOUT	6
LAYOUT RESULT ANALYSIS	6
DC ANALYSIS	6
TRANSIENT ANALYSIS	7
AC ANALYSIS	7
INFERENCE	7
COMMON DRAIN AMPLIFIER	9
SCHEMATIC	9
SCHEMATIC RESULT ANALYSIS	9
DC ANALYSIS	9
TRANSIENT ANALYSIS	10
AC ANALYSIS	10
LAYOUT	11
LAYOUT RESULT ANALYSIS	11
DC ANALYSIS	11
TRANSIENT ANALYSIS	12
AC ANALYSIS	12
INFERENCE	12
COMMON GATE AMPLIFIER	14
SCHEMATIC	14
SCHEMATIC RESULT ANALYSIS	15
DC ANALYSIS	15
TRANSIENT ANALYSIS	15

AC ANALYSIS	16
LAYOUT	16
LAYOUT RESULT ANALYSIS	17
DC ANALYSIS	17
TRANSIENT ANALYSIS	17
AC ANALYSIS	17
INFERENCE	18
DIFFERENTIAL AMPLIFIER	19
SCHEMATIC	19
SCHEMATIC RESULT ANALYSIS	20
TRANSIENT ANALYSIS	20
AC ANALYSIS	20
INFERENCE	20
TEST QUESTION	21
QUESTION	21
SCHEMATIC	21
SCHEMATIC RESULT ANALYSIS	22
TRANSIENT ANALYSIS	22
AC ANALYSIS	22
INFERENCE	23

****All design calculations at the end**


COMMON SOURCE AMPLIFIER

SCHEMATIC

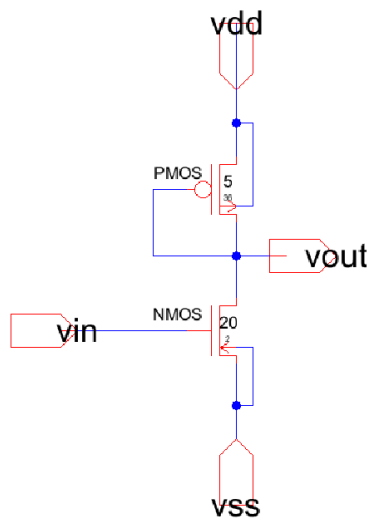


SCHEMATIC RESULT ANALYSIS


DC ANALYSIS

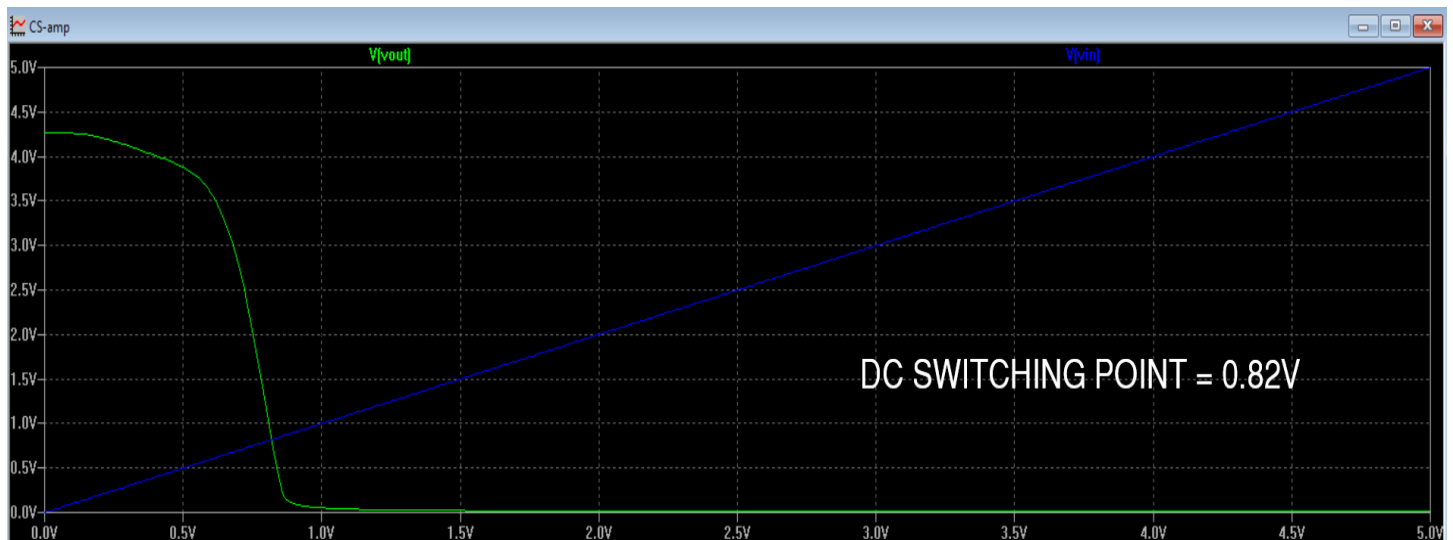


TRANSIENT ANALYSIS

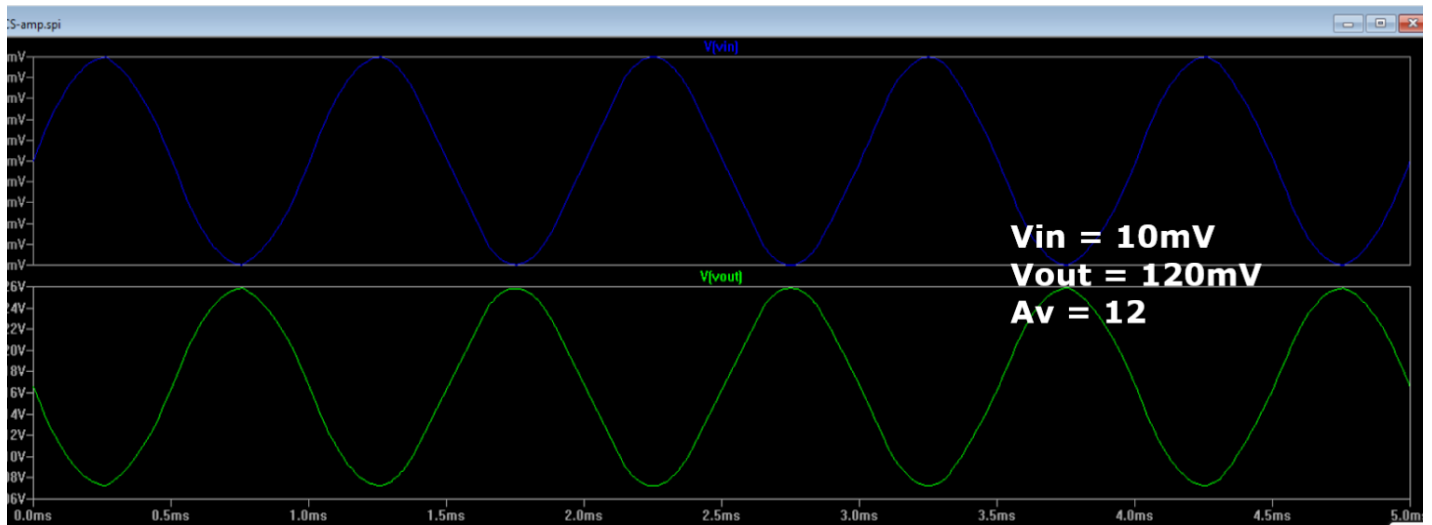

AC ANALYSIS

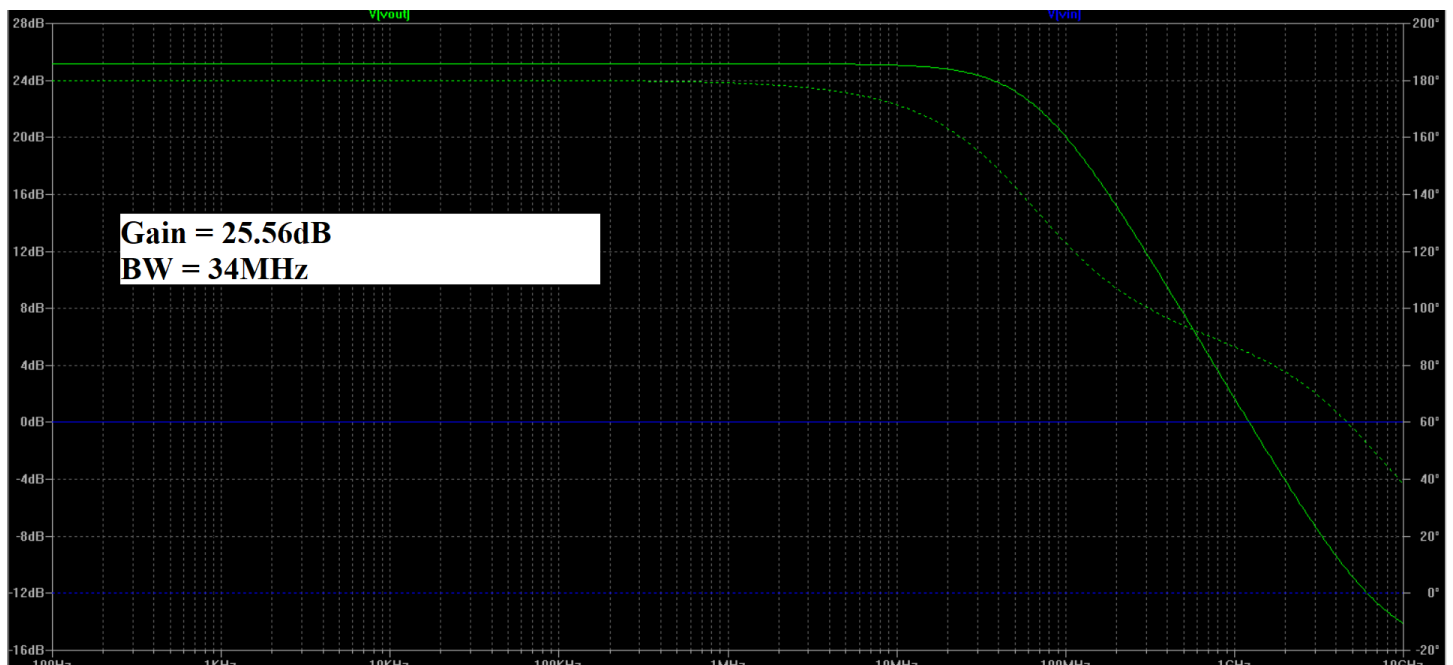


LAYOUT

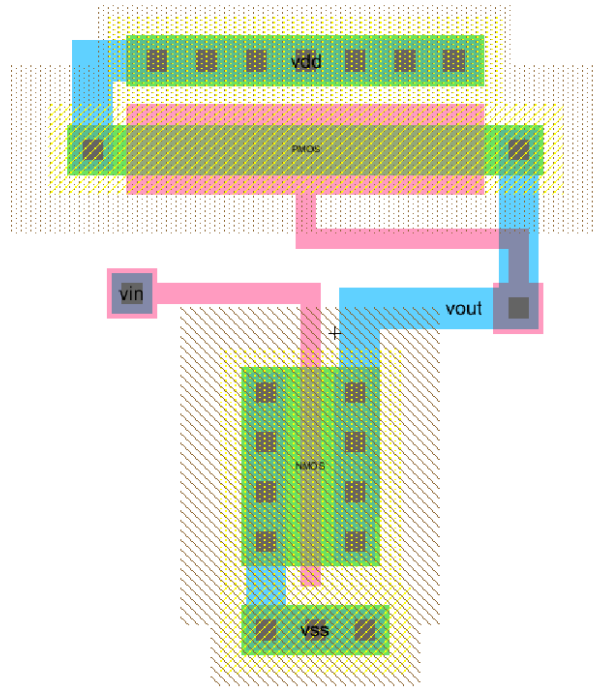


LAYOUT RESULT ANALYSIS


DC ANALYSIS

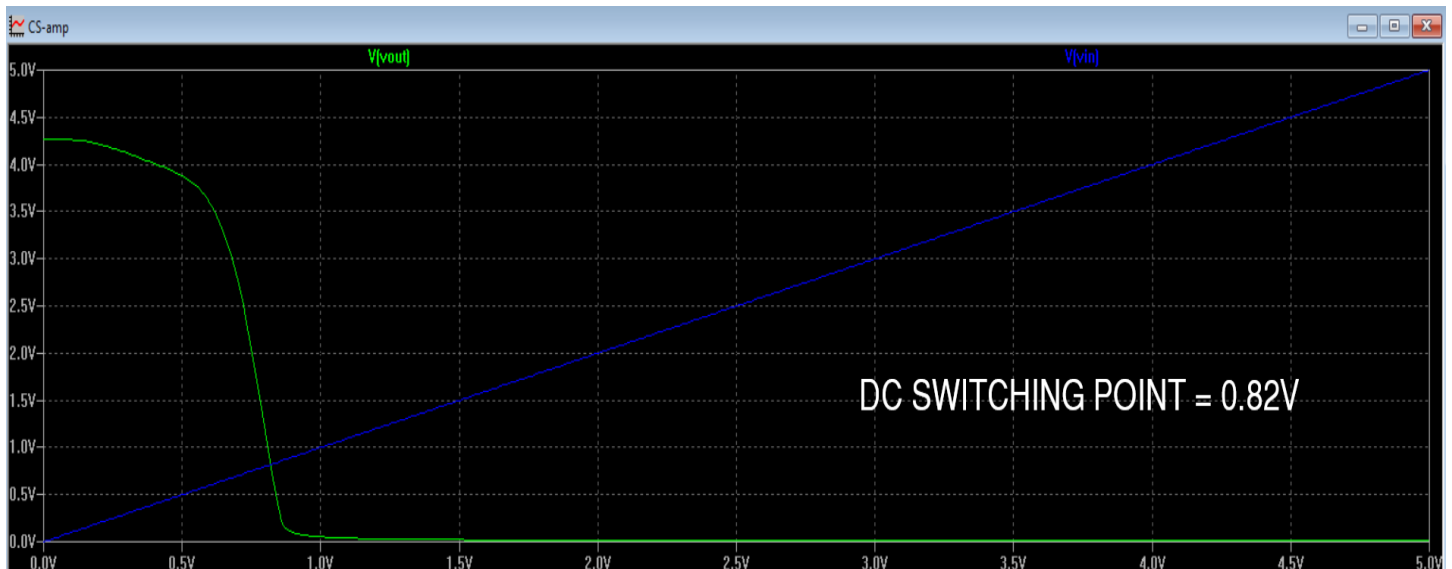

TRANSIENT ANALYSIS

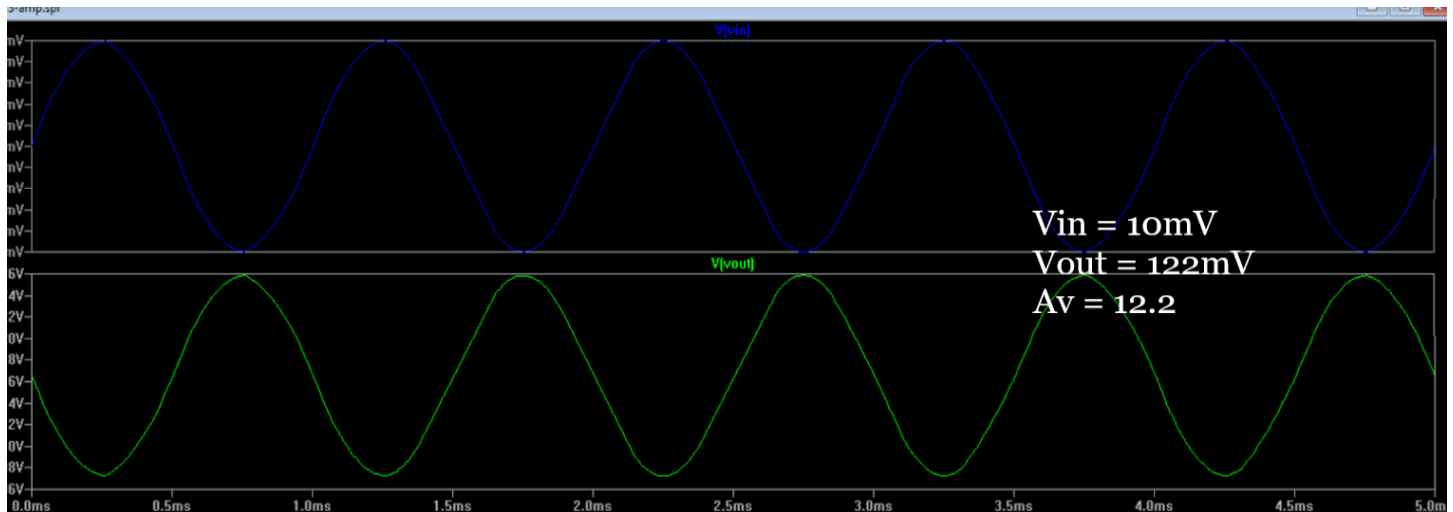

AC ANALYSIS

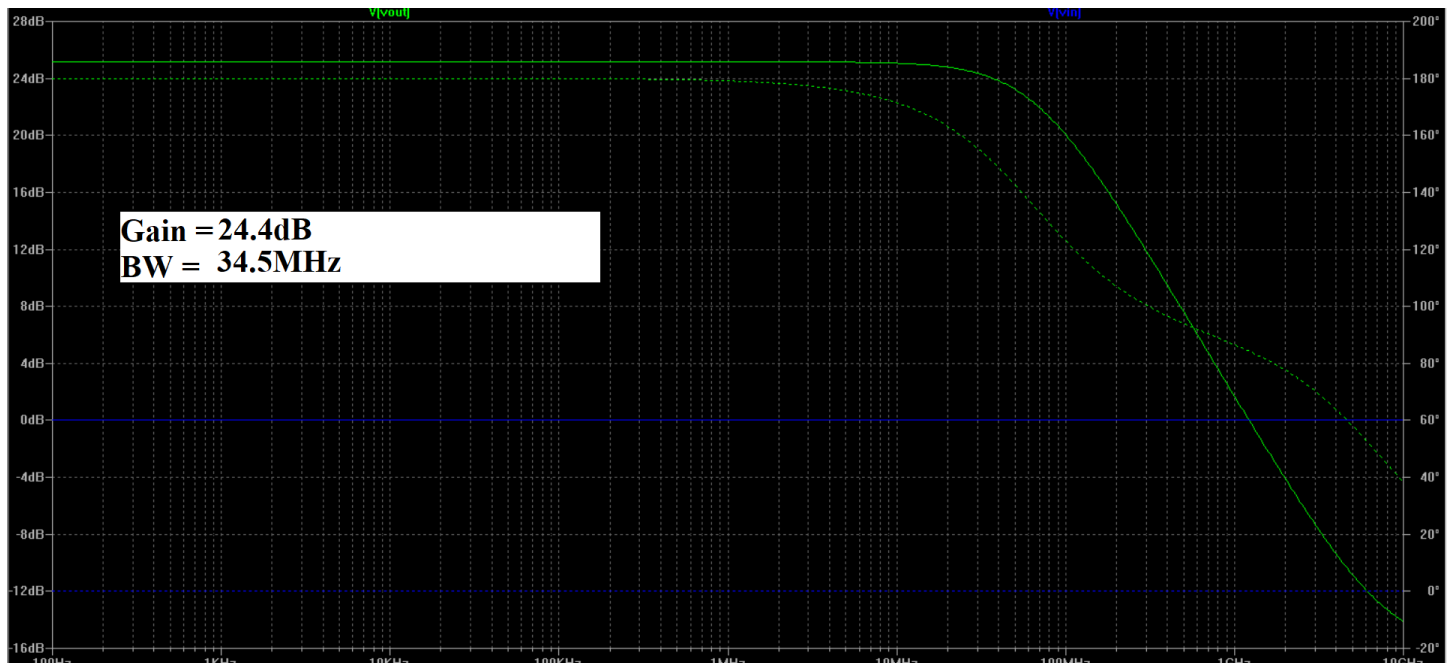

INFERENCE


Designed Gain	12
Designed Gain in db	21.589
Number of transistors	2
$(W/L)_1$	5/36

$(W/L)_2$	20/2
-----------	------

Parameter	Schematic	Layout
DC Switching Point	0.82V	0.82V
Gain from transient analysis	12	12.2
Gain from AC analysis	25.56db	24.4db
Bandwidth	34MHz	34.5MHz


COMMON DRAIN AMPLIFIER

SCHEMATIC

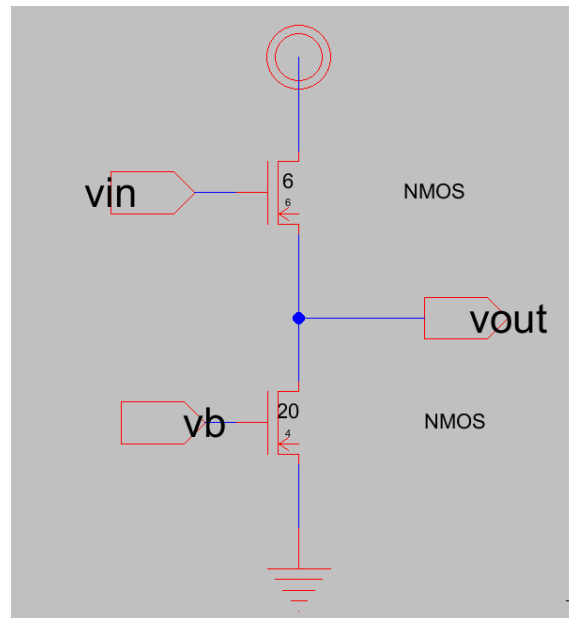


SCHEMATIC RESULT ANALYSIS

DC ANALYSIS

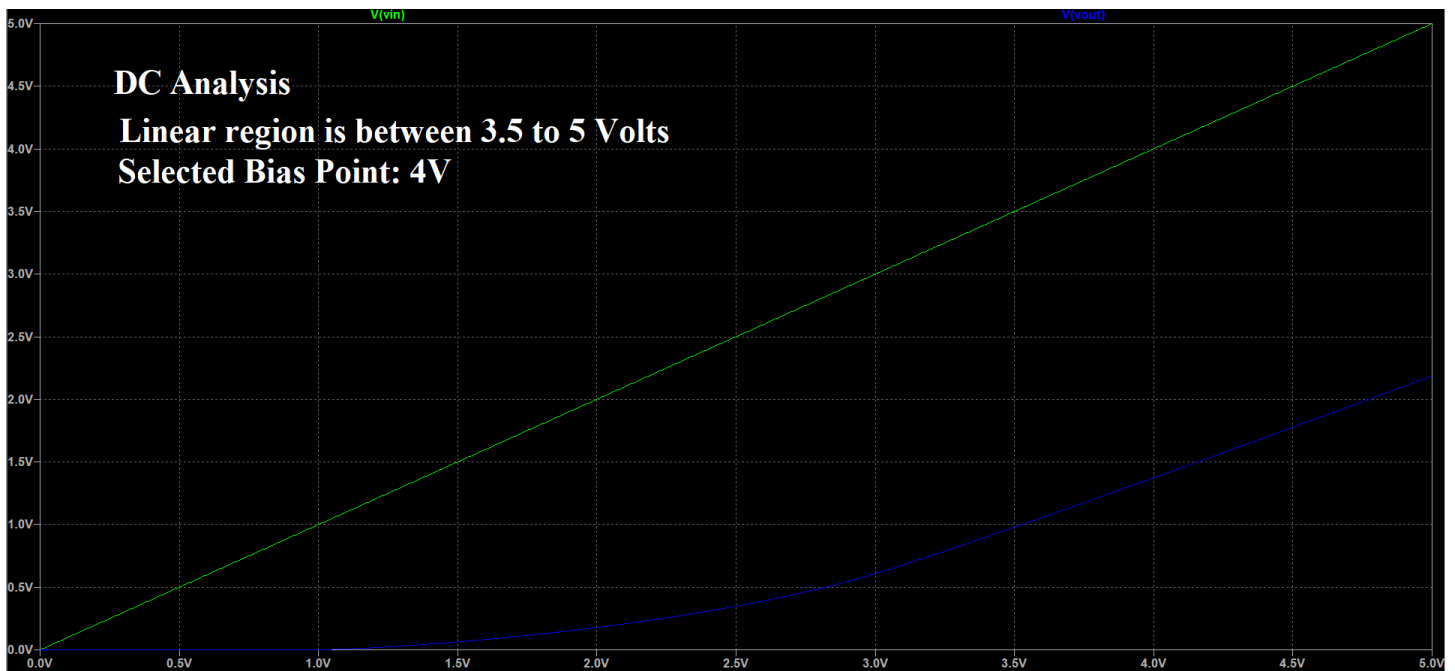


TRANSIENT ANALYSIS

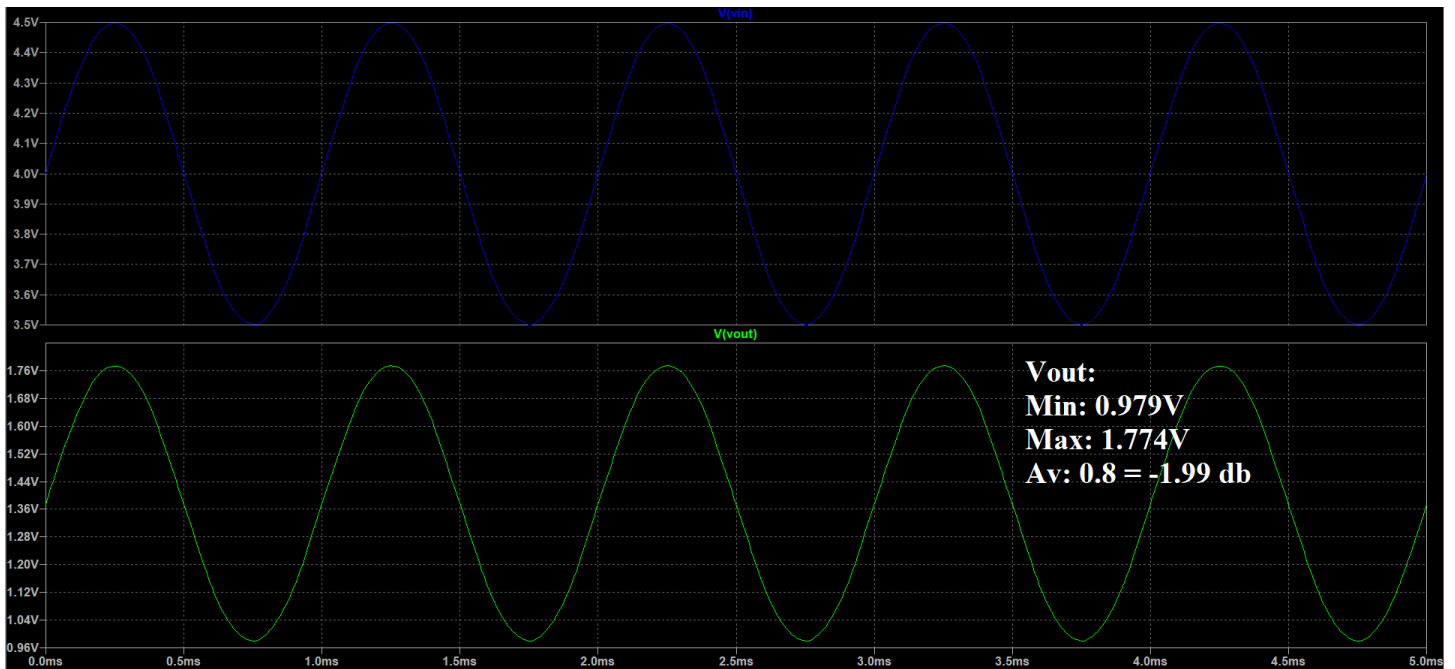

AC ANALYSIS




LAYOUT

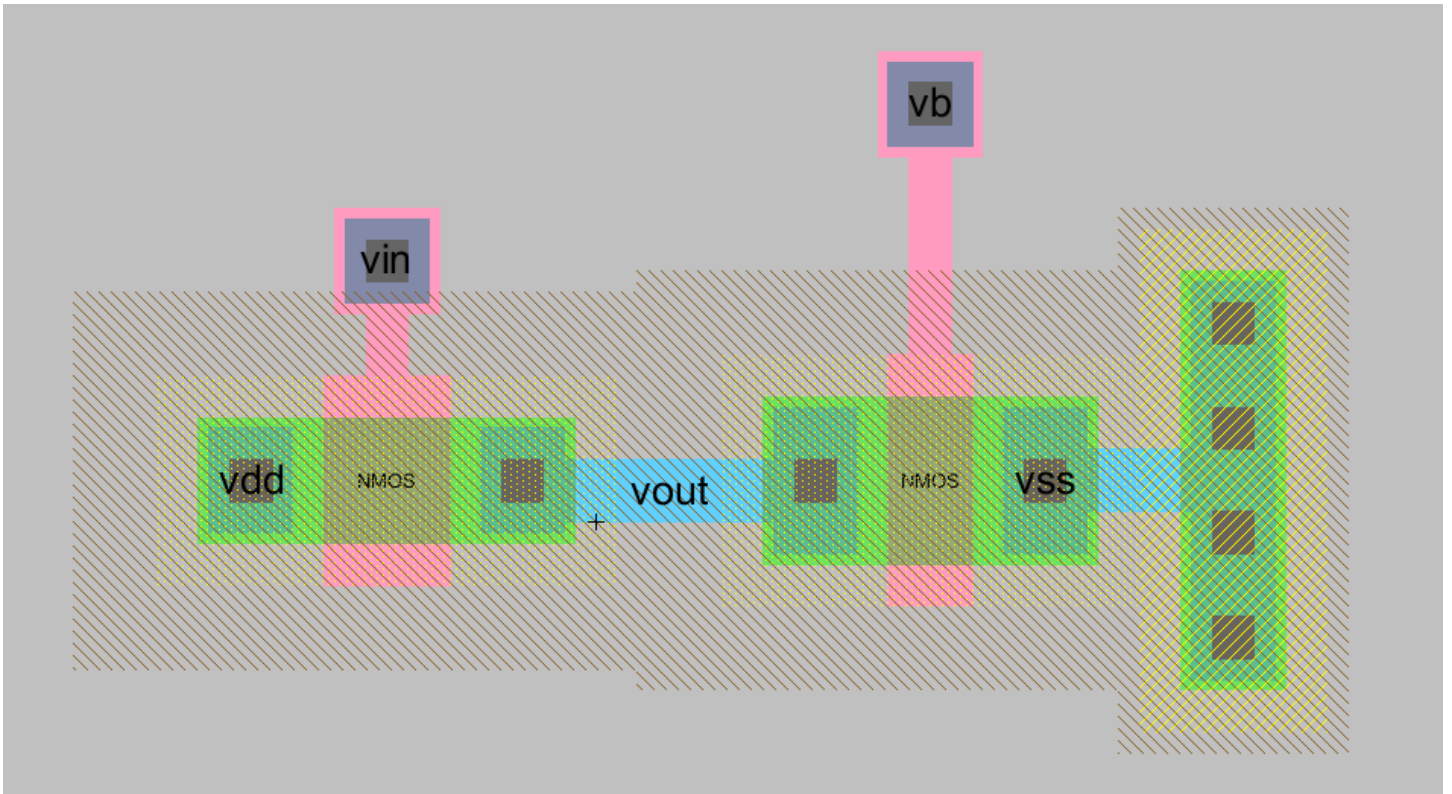


LAYOUT RESULT ANALYSIS


DC ANALYSIS

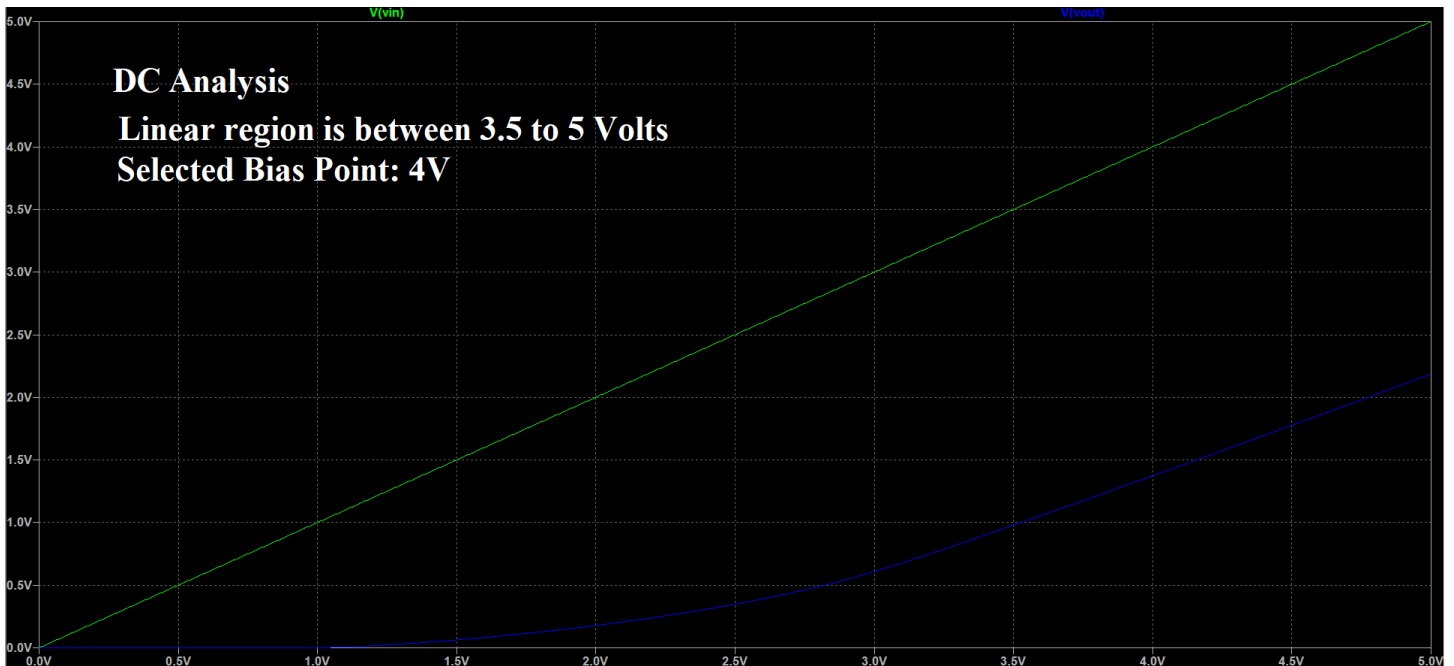

TRANSIENT ANALYSIS

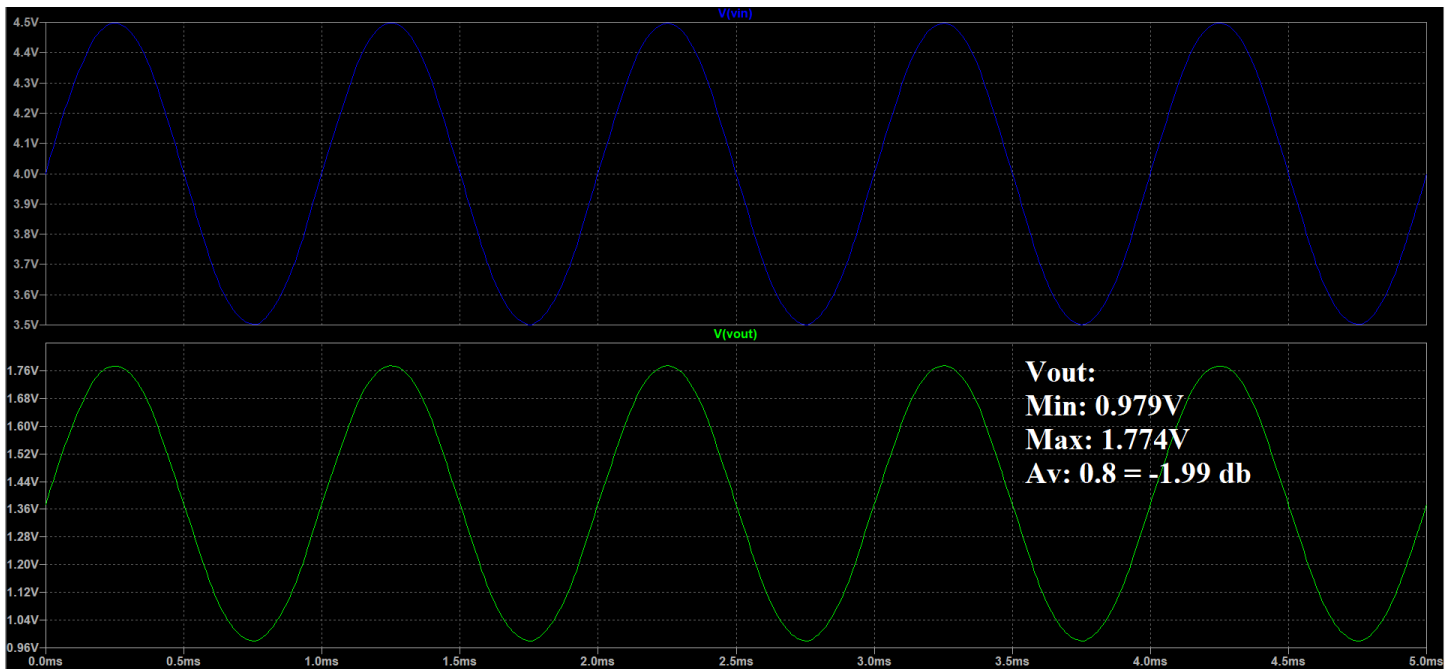

AC ANALYSIS

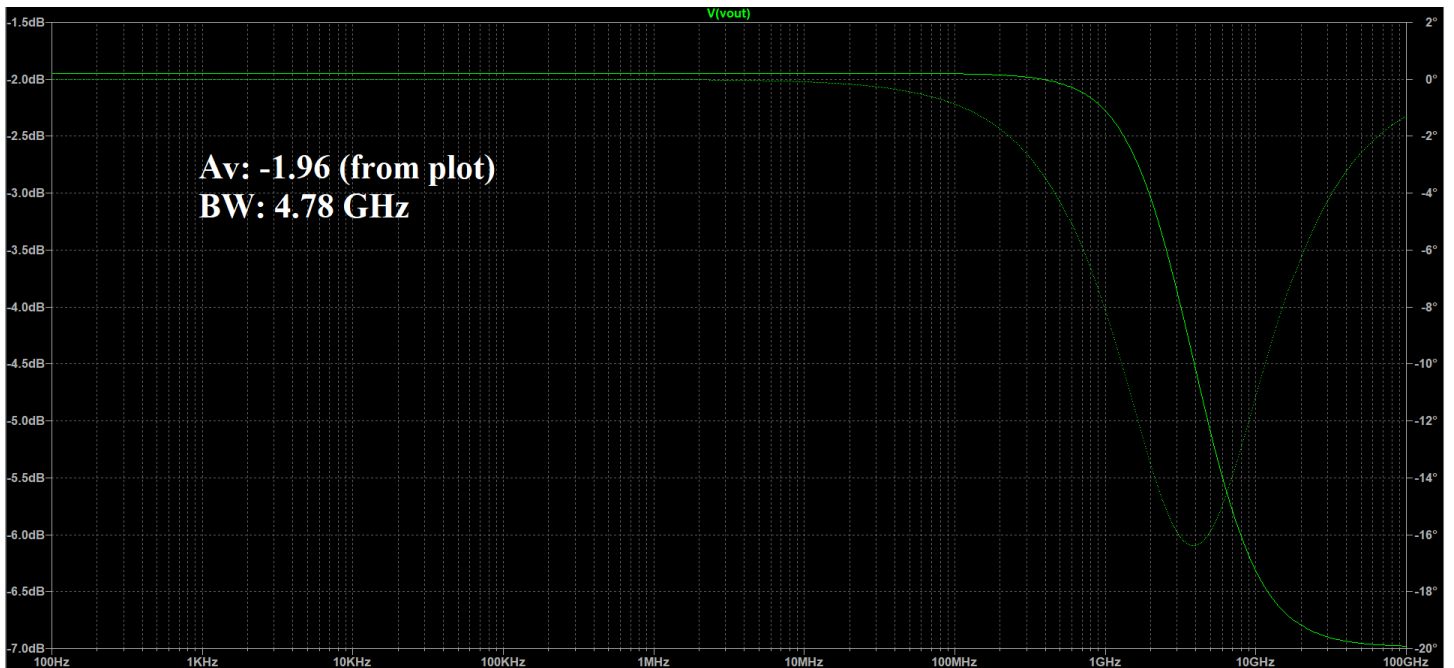

INFERENCE


Designed Drain Current	0.35 mA
Obtained Gain	0.84
Number of transistors	2

$(W/L)_1$	6:6
$(W/L)_2$	2/1

Parameter	Schematic	Layout
DC Switching Point	.8v	.8v
Gain from transient analysis	1	0.9
Gain from AC analysis	-1.5db	-1.5db
Bandwidth	4.78Ghz	4.78Ghz


COMMON GATE AMPLIFIER

SCHEMATIC

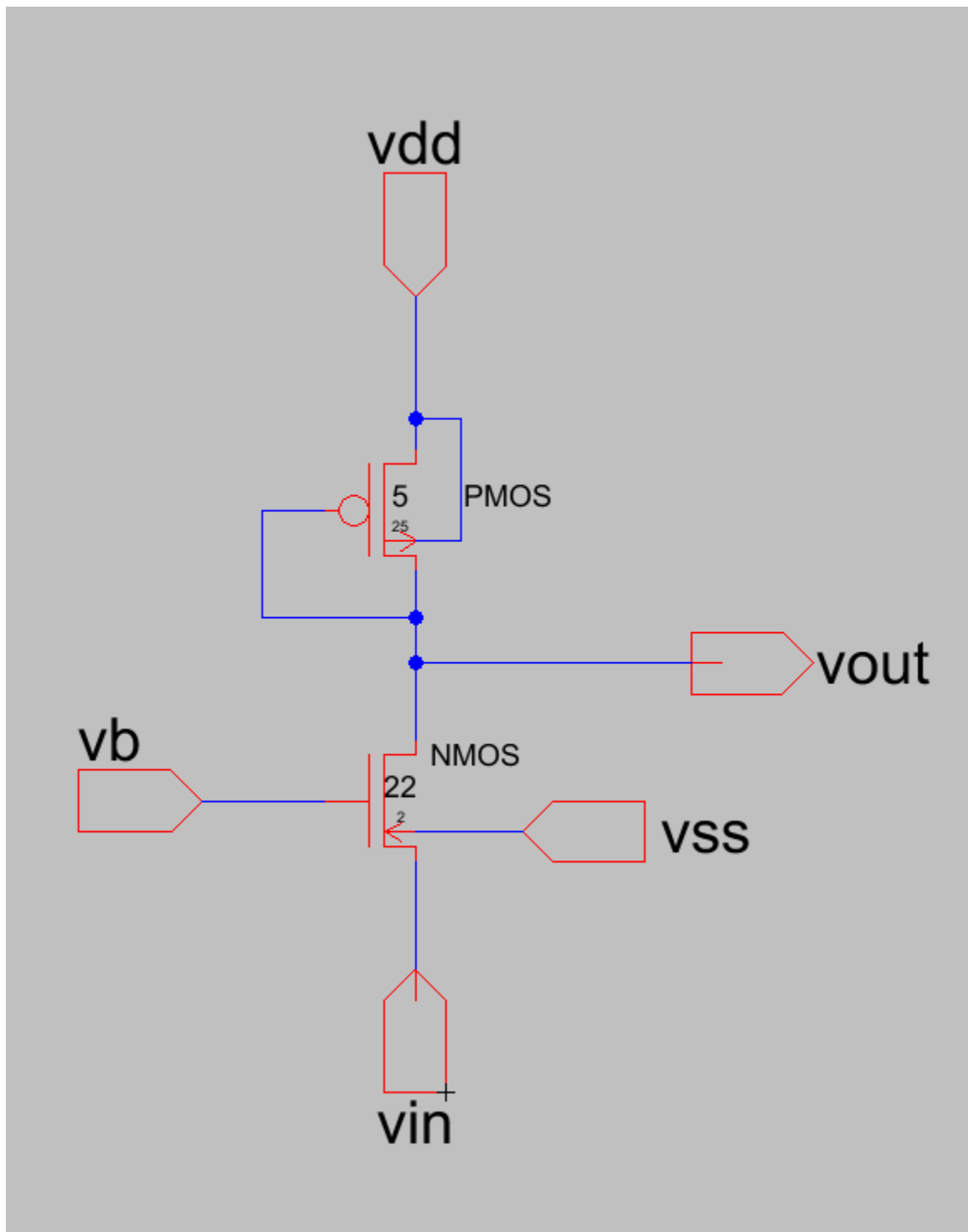


SCHEMATIC RESULT ANALYSIS

DC ANALYSIS

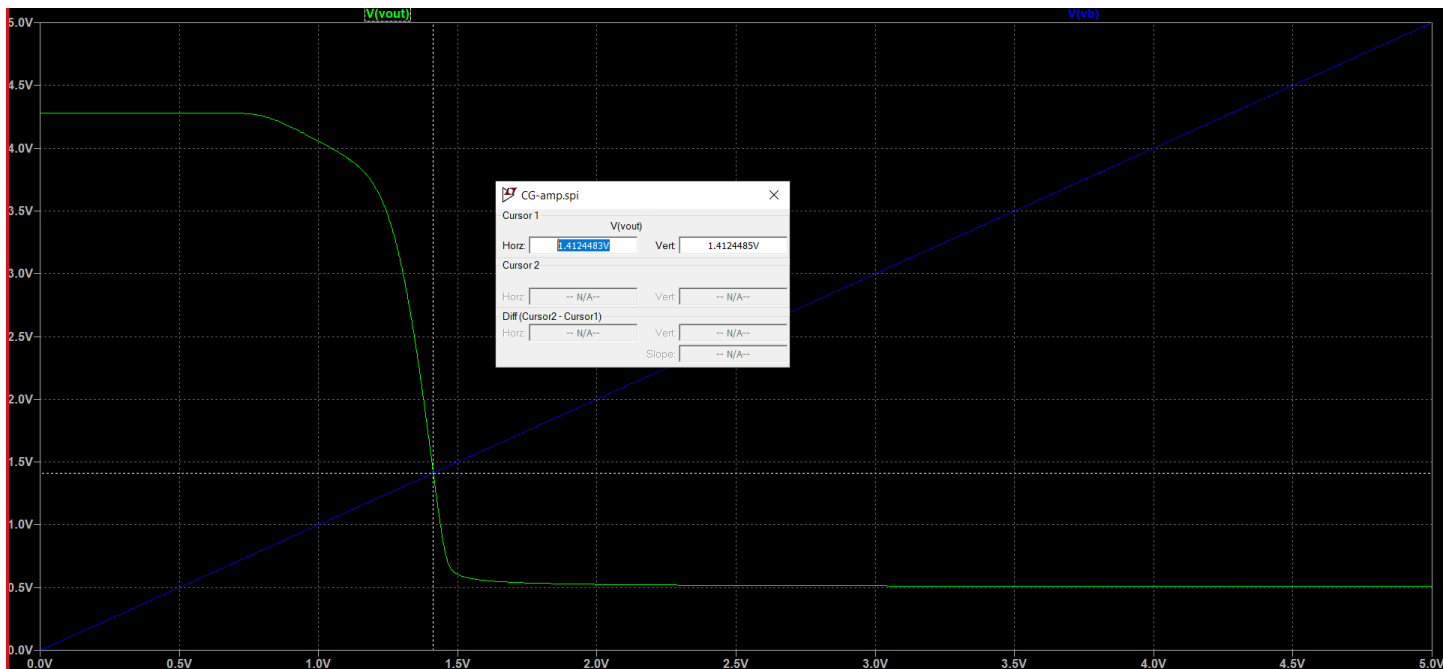


TRANSIENT ANALYSIS

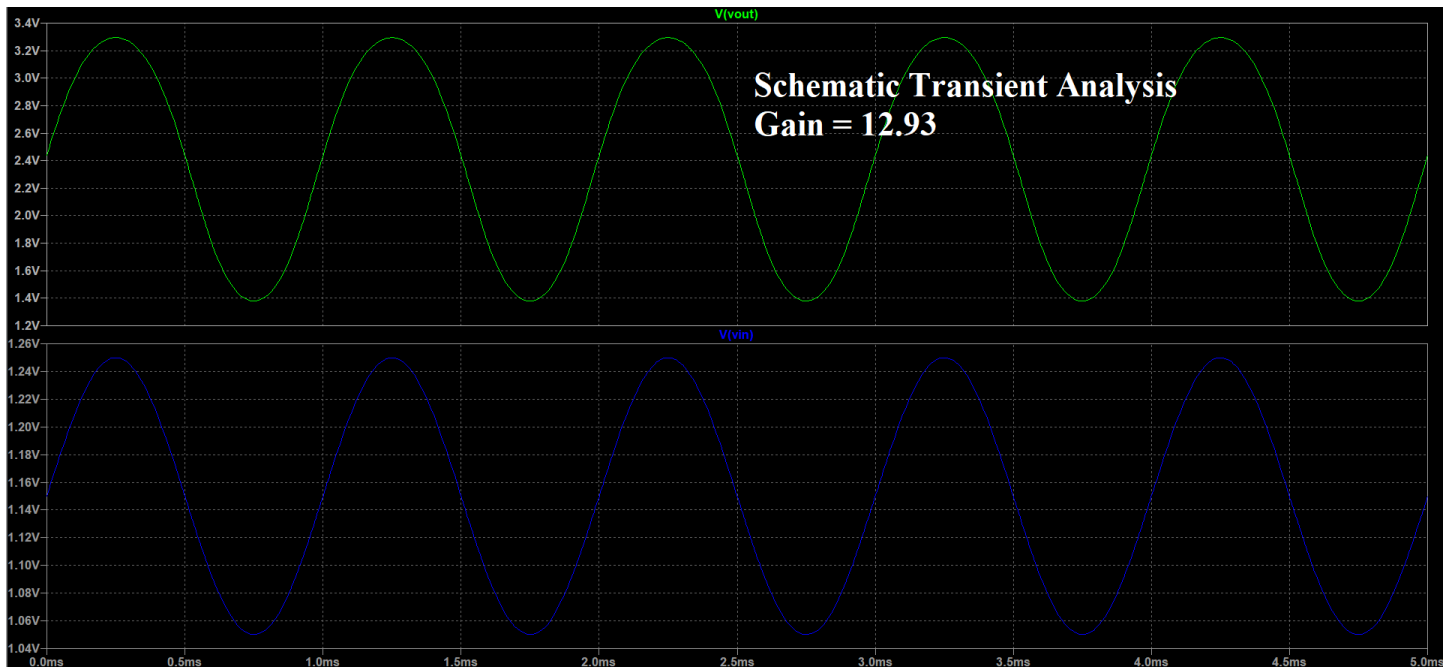

AC ANALYSIS



LAYOUT

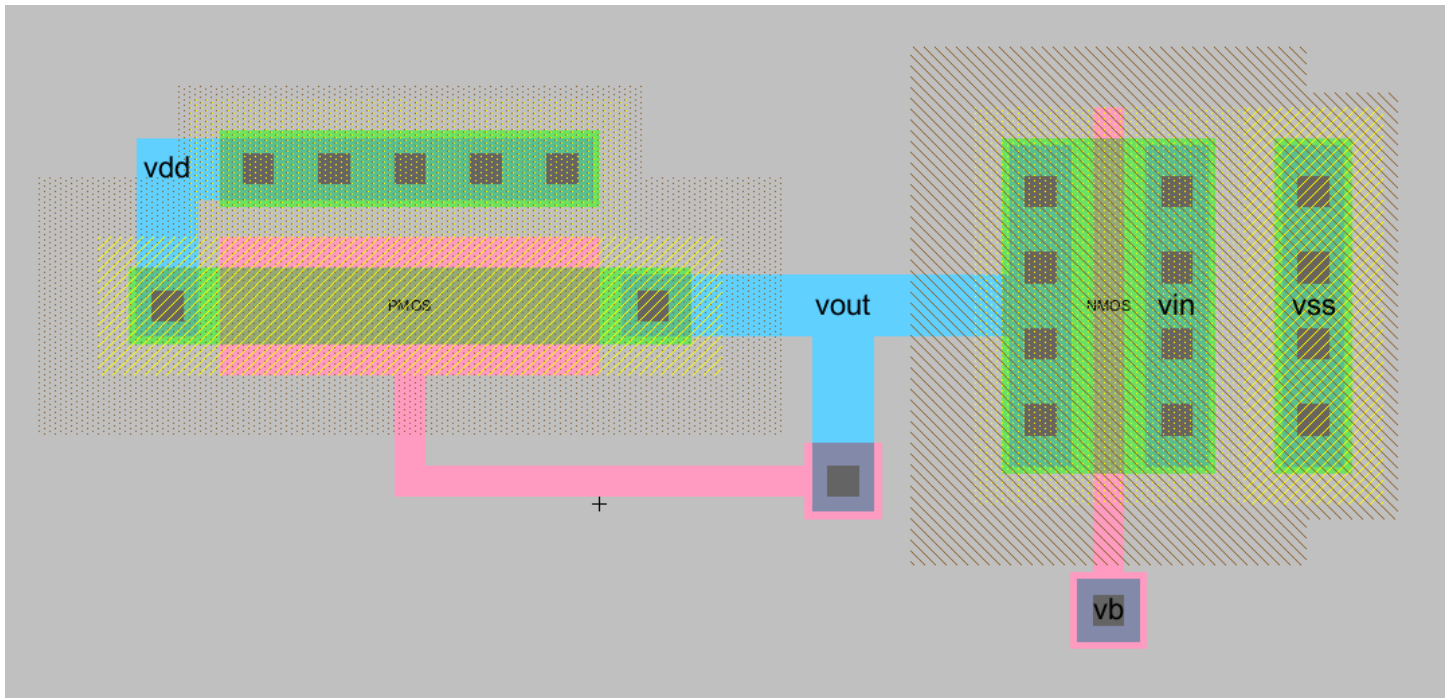


LAYOUT RESULT ANALYSIS


DC ANALYSIS



TRANSIENT ANALYSIS

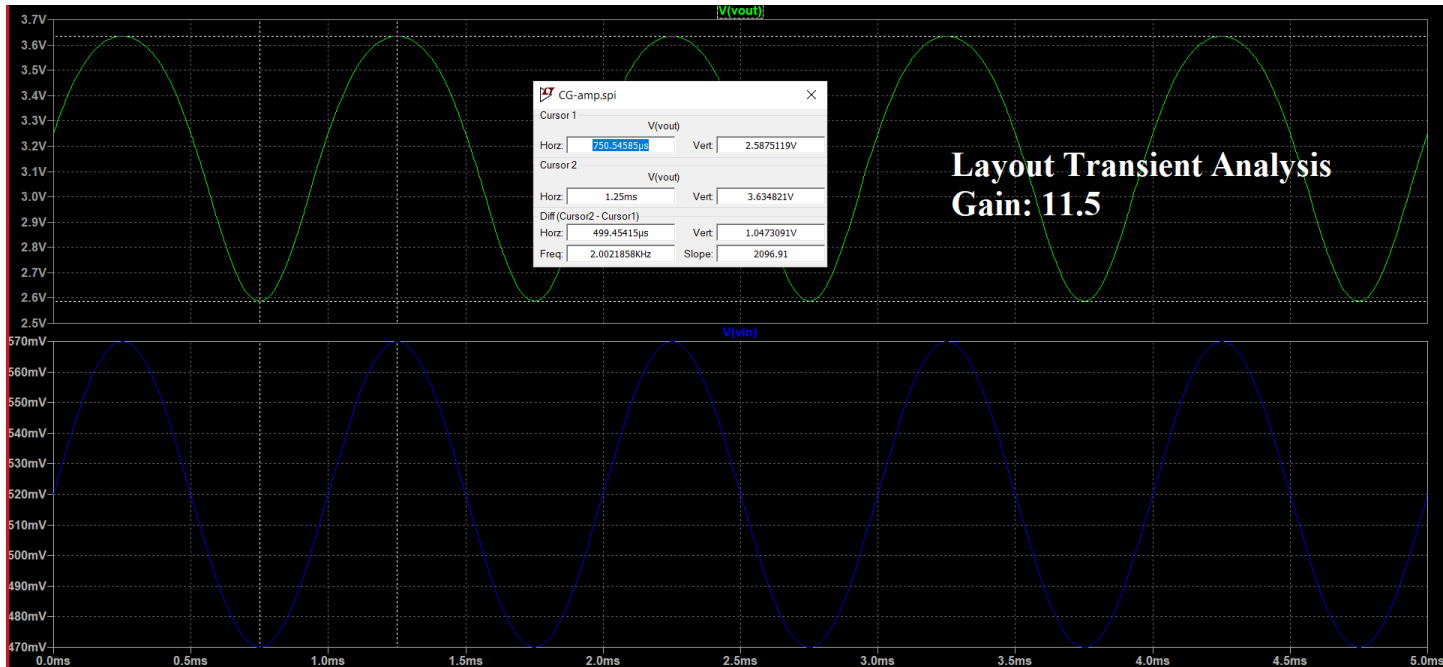

AC ANALYSIS

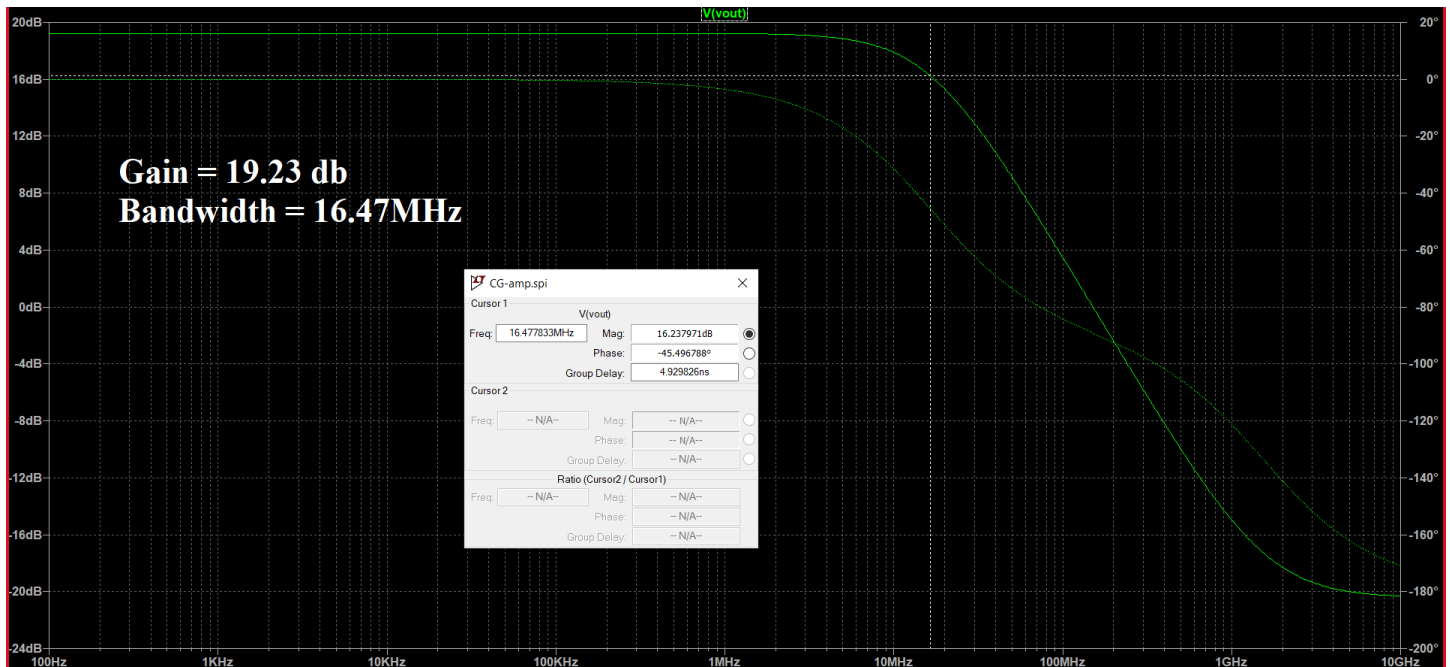


INFERENCE

Designed Gain	13
Designed Gain in db	22.27db
Number of transistors	2
$(W/L)_1$	11/1
$(W/L)_2$	5/25

Parameter	Schematic	Layout
DC Switching Point	1.42	1.41
Gain from transient analysis	12.97	11.55
Gain from AC analysis	22.25 db	21.25 db
Bandwidth	160 MHz	16.4 MHz


DIFFERENTIAL AMPLIFIER

SCHEMATIC

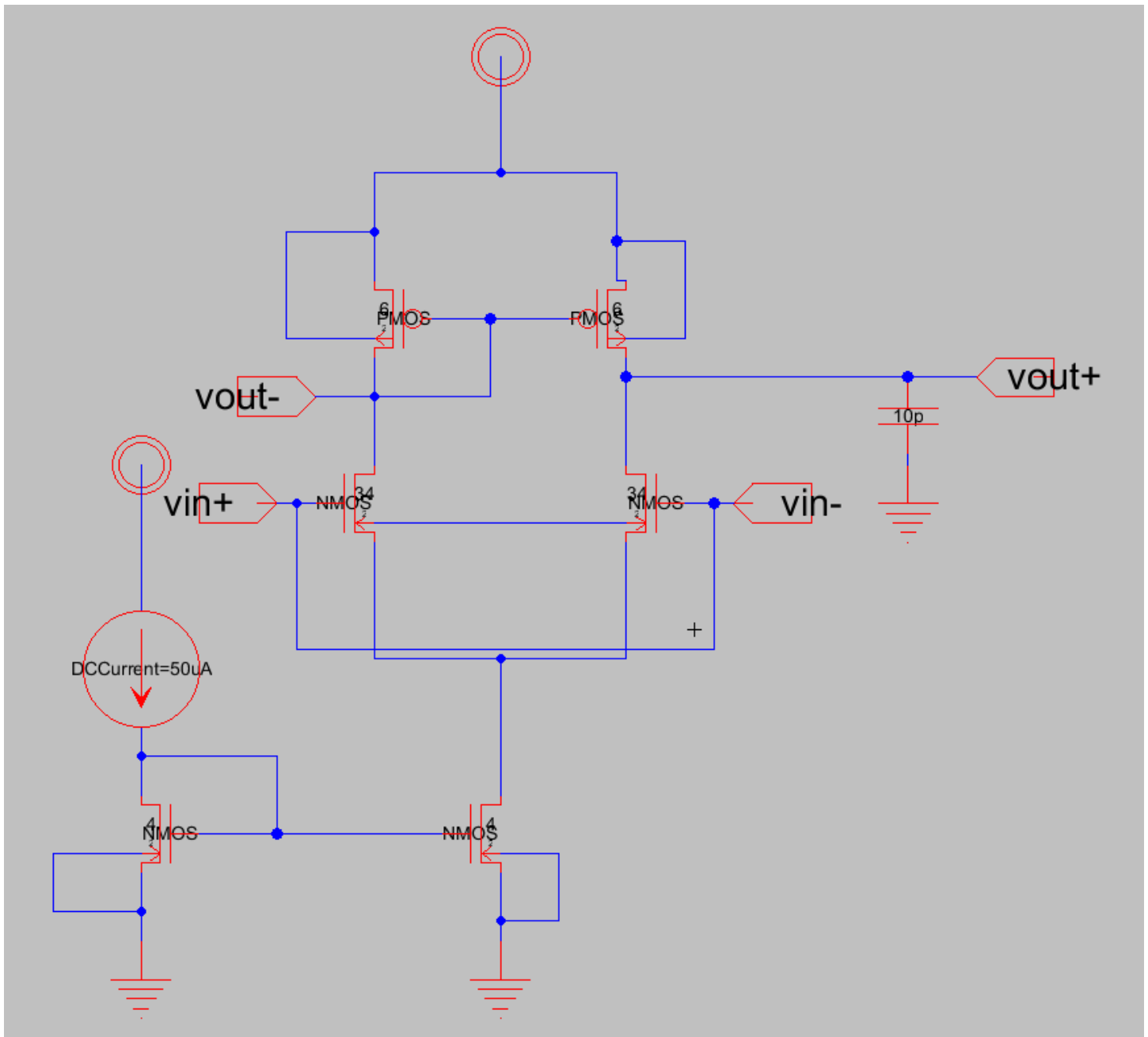

SCHEMATIC RESULT ANALYSIS

TRANSIENT ANALYSIS

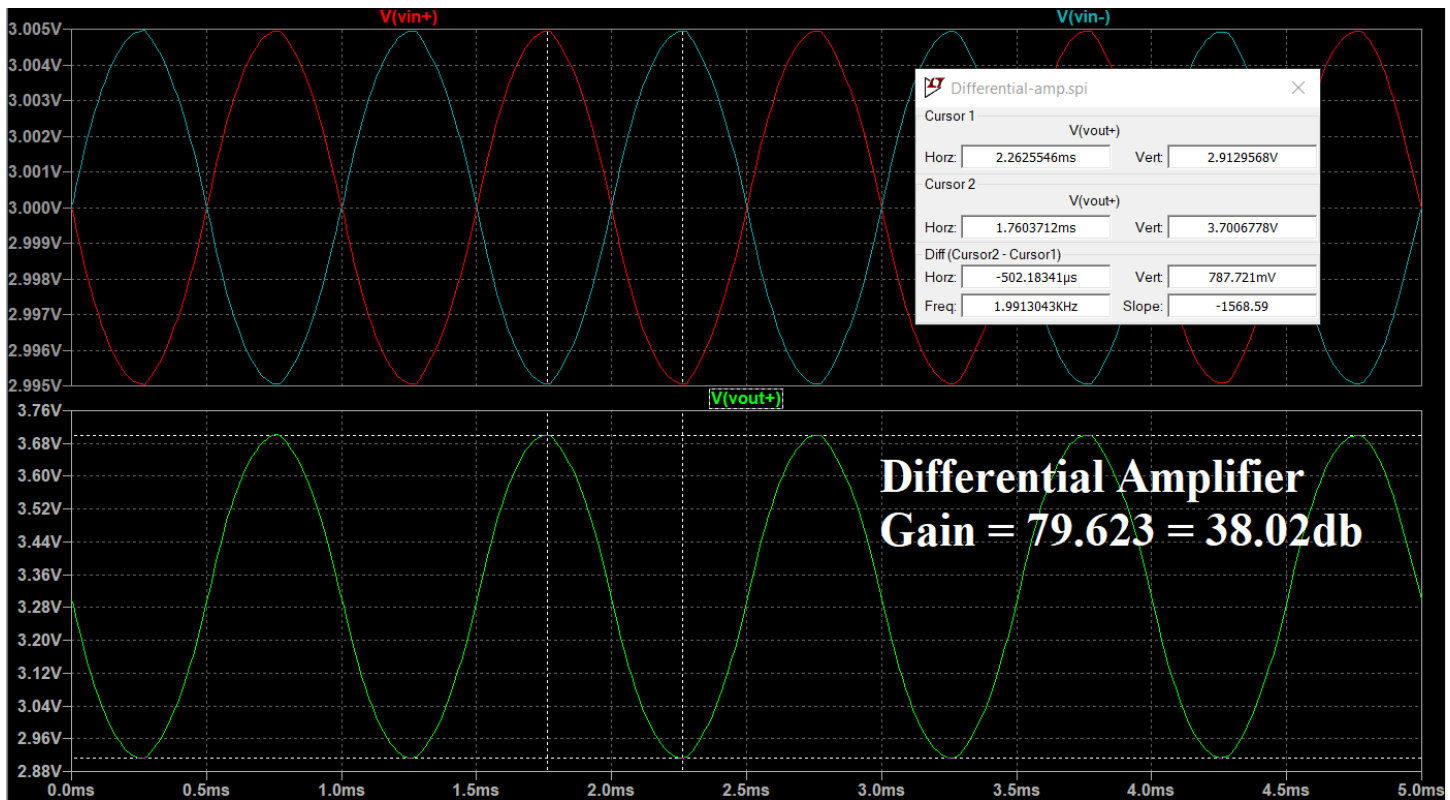

AC ANALYSIS

INFERENCE

Designed Gain	100
Designed Gain in db	40 db
Number of transistors	6
$(W/L)_1 = (W/L)_2$	17/1
$(W/L)_3 = (W/L)_4$	6/2
$(W/L)_5 = (W/L)_8$	4/2


TEST QUESTION

QUESTION

Design an Operational Amplifier for a gain of 35db and simulate the same using electric tool.


Given gain: **35db**

SCHEMATIC

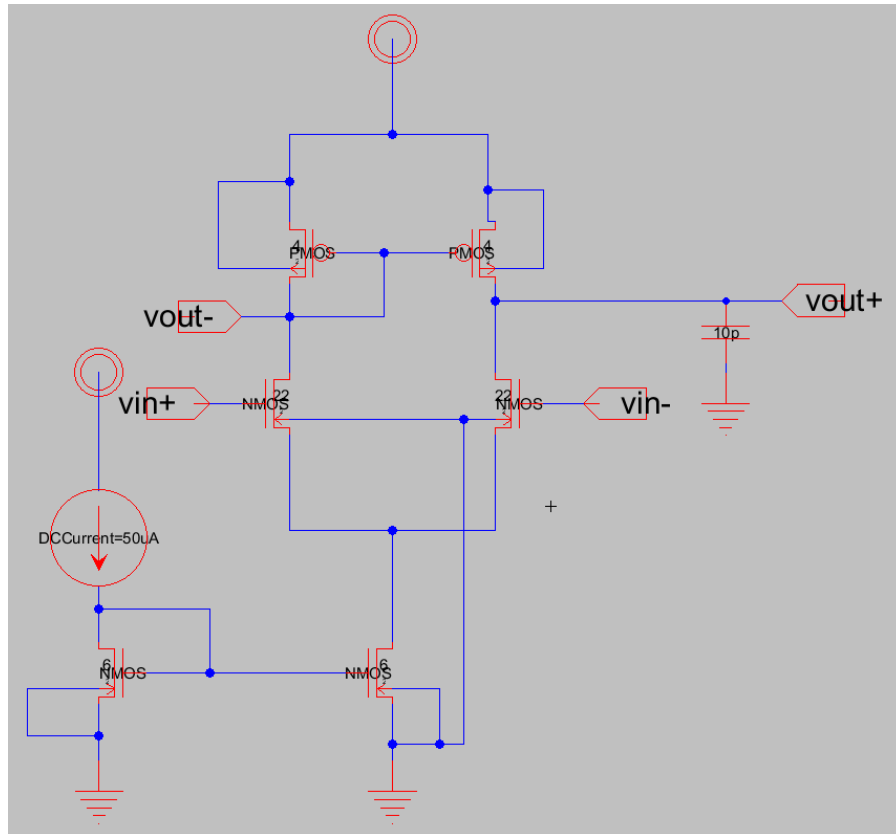


SCHEMATIC RESULT ANALYSIS

TRANSIENT ANALYSIS

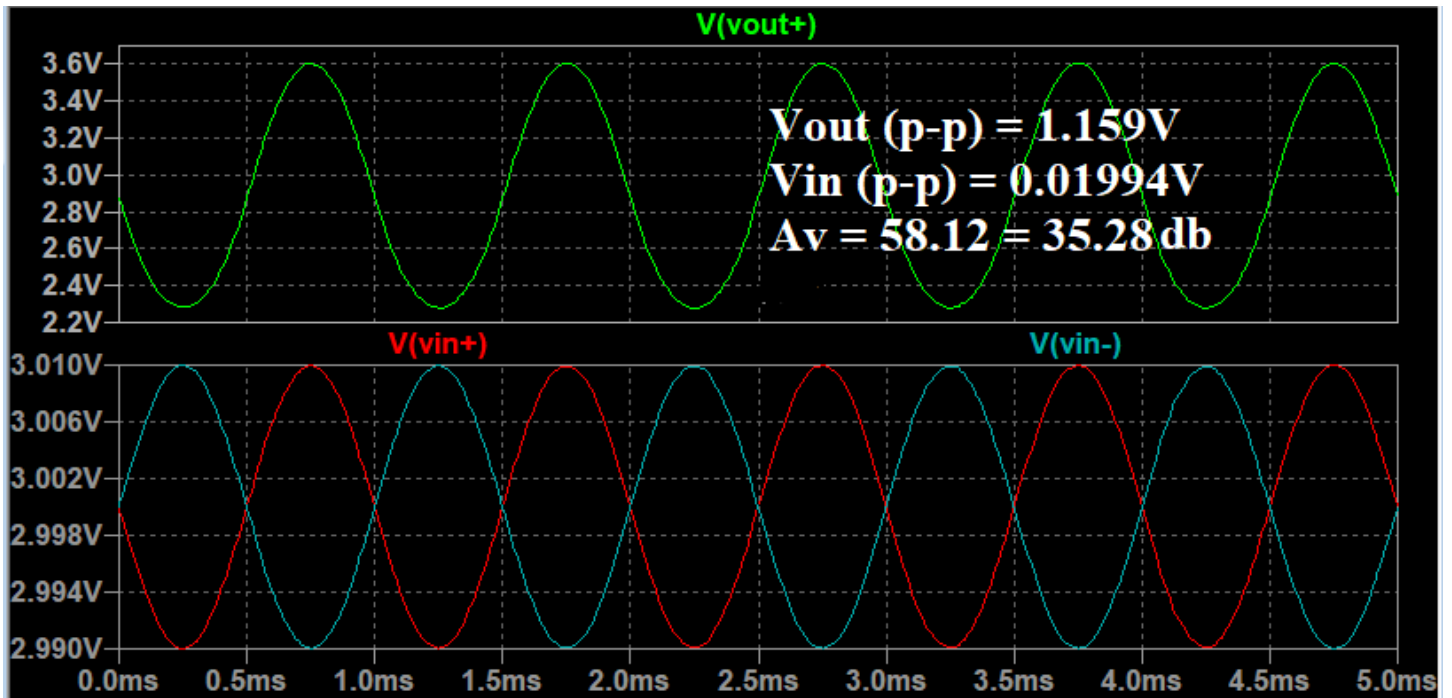

AC ANALYSIS

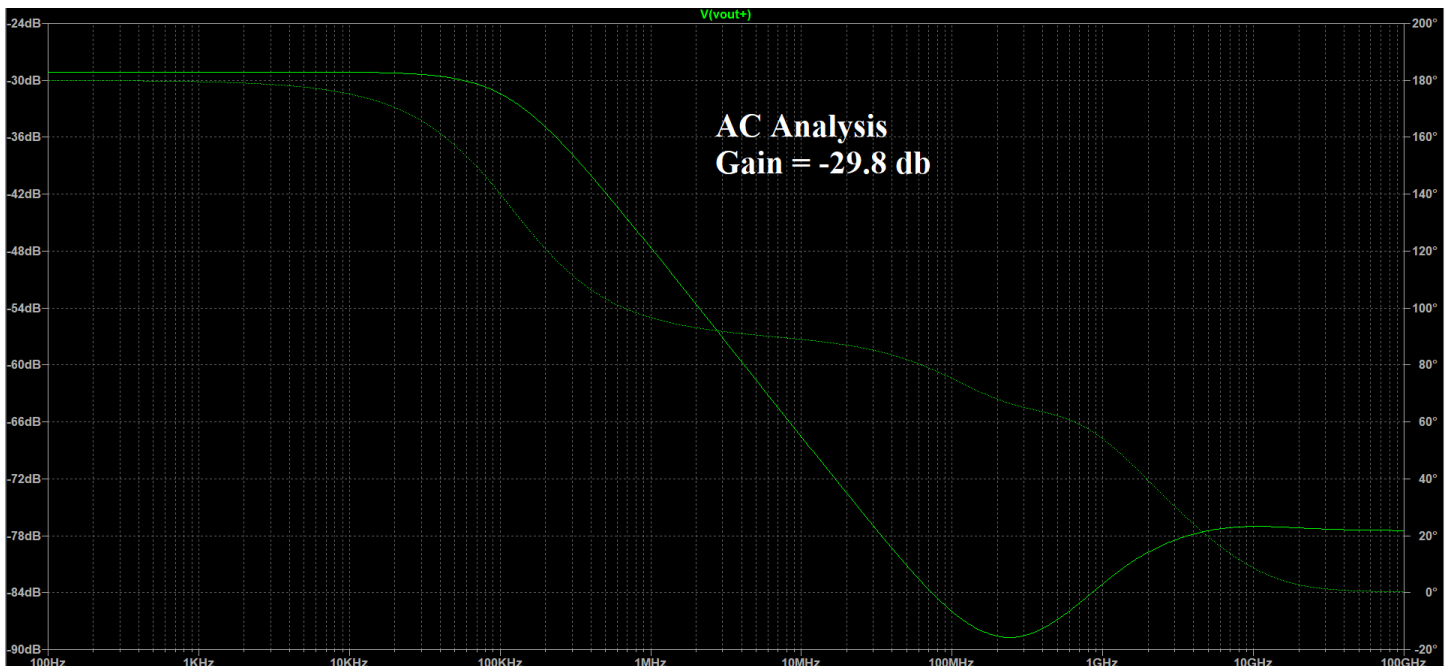


INFERENCE

Designed Gain	56.23
Designed Gain in db	35 db
Number of transistors	6
$(W/L)_1 = (W/L)_2$	11.1 ~ 12
$(W/L)_3 = (W/L)_4$	1.57 ~ 2
$(W/L)_5 = (W/L)_8$	2.43 ~ 3
Obtained Gain	58.12
Obtained Gain in db	35.28

Common Source Amplifier:

$$A_{v1} = -g_{m1} \frac{R_d}{M_2}$$

$$R_d \approx \frac{1}{g_{m2}}$$

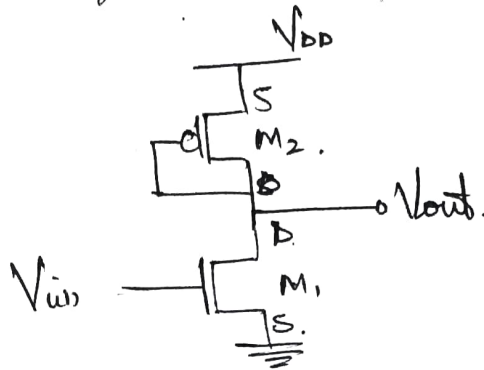

$$A_{v1} = -\left(\frac{g_{m1}}{g_{m2}}\right) = -\left(\frac{\sqrt{2 \mu_n C_{ox} (W/L)_1 I_{D1}}}{\sqrt{2 \mu_p C_{ox} (W/L)_2 I_{D2}}}\right)$$

$$\mu_n = 2 \mu_p$$

$$A_{v1} = -\left(\frac{\sqrt{2 \mu_n C_{ox} (W/L)_1 I_{D1}}}{\sqrt{2 \mu_p C_{ox} (W/L)_2 I_{D2}}}\right) = -\left(\frac{2 (W/L)_1}{(W/L)_2}\right)^{1/2}$$

$$(A_{v1})^2 = \frac{-2 (W/L)_1}{(W/L)_2} \left| \frac{(W/L)_1}{(W/L)_2} = \frac{(A_{v1})^2}{2} \right.$$

For a gain ≈ 8 :

$$A_{v1} \approx 8$$

Taking $(W/L)_1 = \frac{6}{1}$

$$\frac{(W/L)_1}{(W/L)_2} = \frac{6}{2} = \frac{8 \times 8}{2}$$


$$(W/L)_2 = \frac{6 \times 7}{8 \times 2} = \frac{3 \times 7}{8 \times 2} = \frac{3}{16}$$

Min width

$$P_{min} \approx 2$$

we take 3

Common Drain Amplifier:

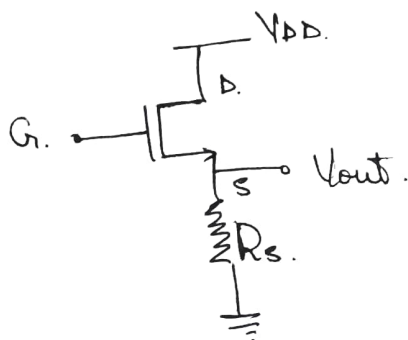

$$A_v = \frac{g_m r_{o1}}{1 + (g_m + g_{mb}) r_{o1}}$$

$g_m \rightarrow$ Transconductance


$g_{mb} \rightarrow$ body Transconductance

$$A_v \approx \frac{g_m}{g_m + g_{mb}}$$

Input $z \rightarrow$ very high.

O/P $z \rightarrow$ low

• Used to prevent loading effect.

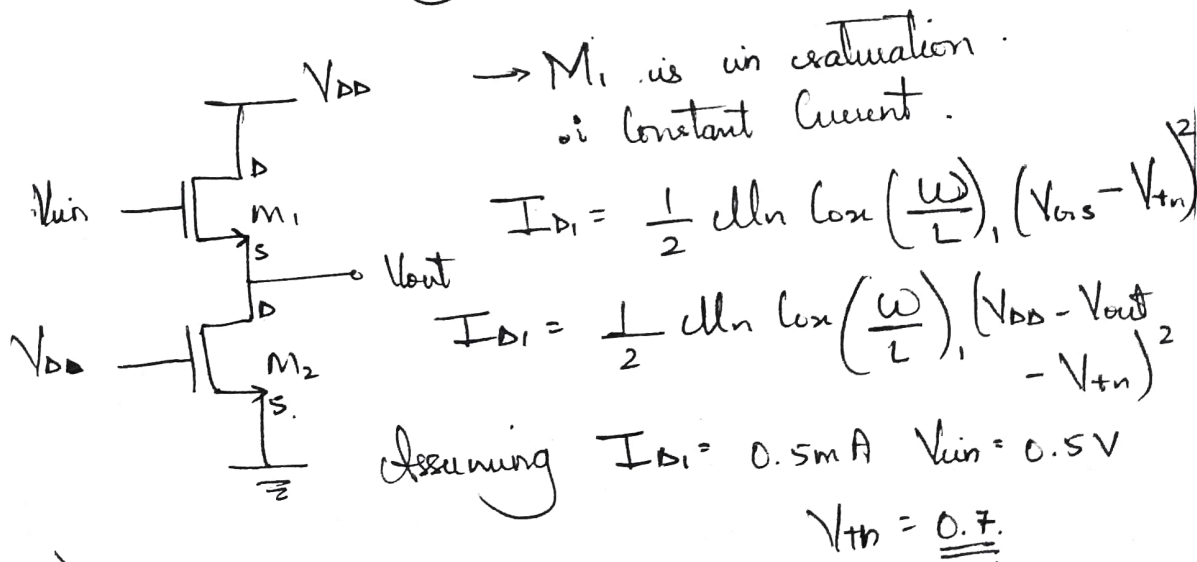

$$\left(\frac{W}{L} \right)_1 = 1 = \frac{6}{6}$$

$$C_{ox} = \frac{\epsilon_a \epsilon_{ox}}{t_{ox}} = \frac{3.9 \times 8.854 \times 10^{-12}}{1.39 \times 10^{-8}}$$

$$V_{th} = \underline{\underline{0.6696 \text{ V}}}$$

$$C_{ox} = \underline{\underline{2.484 \times 10^{-3} \text{ F}}}$$

$$\mu_n = 458.43 = \underline{\underline{0.045843 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}}}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{out} - V_{tn})^2$$

$$(V_{DD} - V_{out} - V_{tn})^2 = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1}}$$

$$V_{out} = V_{DD} - V_{tn} - \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1}}$$

$$V_{out} = \underline{\underline{1.3366 \text{ V.}}}$$

$$M_2 \text{ also in saturation} \therefore V_{DS} = V_{GS} - V_{t}$$

$$V_{DS2} = V_b - V_{th.} = \underline{\underline{V_{out.}}}$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (V_{out})^2$$

$$\left(\frac{W}{L} \right)_2 = \underline{\underline{4.920}} = \underline{\underline{5}}$$

$$W_2 = 20.$$

$$L_2 = \underline{\underline{4.}}$$

For a drain current $I_{DS} = \underline{\underline{0.35 \text{ mA}}}$.

$$V_{in} = 0.5 \text{ V.}$$

$$V_{th} = 0.7 \text{ V.}$$

$$C_{ox} = 2.484 \times 10^{-3} \text{ F}$$

$$\mu_n = 0.045843 \text{ m}^2/\text{Vs}$$

$$\left(\frac{w}{L}\right)_1 = \frac{6}{6} = 1$$

$$\textcircled{1} V_{out} = V_{DD} - V_{th} - \sqrt{\frac{2 I_{DS}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_1}}$$

$$V_{out} = 5 - 0.7 - \sqrt{\frac{2 \times 0.35 \times 10^{-3}}{0.045843 \times 2.484 \times 10^{-3} \times 1}}$$

$$\boxed{V_{out} = 1.8206 \text{ V.}}$$

$$\textcircled{2} \left(\frac{w}{L}\right)_2 = \frac{2 I_{DS}}{\mu_n C_{ox} (V_{out})^2} = \frac{2 \times 0.35 \times 10^{-3}}{0.045843 \times 2.484 \times 10^{-3} \times (1.82)^2}$$

$$\left(\frac{w}{L}\right)_2 = 1.85 = \frac{37}{20} \approx \frac{19}{10} \approx \boxed{\frac{4}{2}}$$

$$V_{in} = \underline{\underline{1}}$$

$$V_{out} = 1.774 - 0.979 \times 0.8 = \cancel{1.99 \text{ dB}}$$



$$A_v = \frac{V_{out}}{V_{in}} = 0.8 = \underline{\underline{-1.99 \text{ dB}}}$$

From AC-analysis. (Plot).

$$A_v = -1.95 \text{ dB.}$$

$$BW = \underline{\underline{4.78 \text{ GHz}}}$$

Common Gate Amplifier.

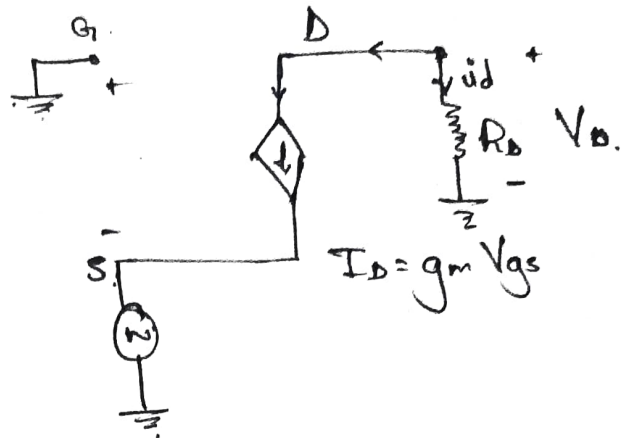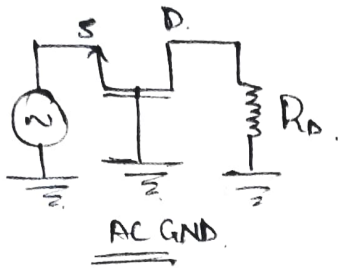

- Low input Impedance
- High o/p — " —
- LNA

$$I_o + I_D = 0.$$


$$I_o = \frac{V_o}{R_D} = -I_D = -g_m V_{gs}.$$

$$\frac{C_o}{R_D} = -g_m (V_{in}).$$

$$V_{gs} = -V_{in}$$

$$\frac{C_o}{C_{in}} = \underline{g_m R_D}. \quad \therefore \text{No change in phase.}$$

$$R_D \approx \frac{1}{g_{m2}}.$$

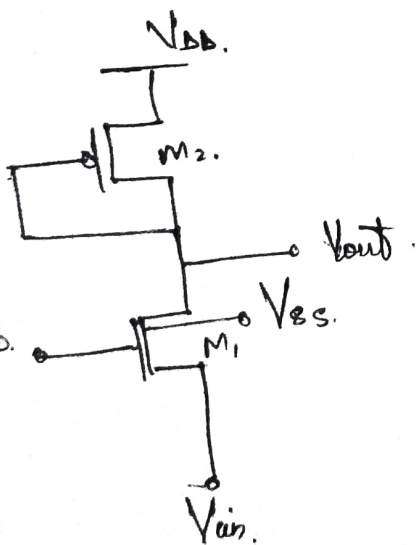


$$A_v = \frac{g_{m1}}{g_{m2}}.$$

$$A_{v1} = \left(\frac{2 \left(\frac{W}{L} \right)_1}{\left(\frac{W}{L} \right)_2} \right).$$

$$\text{Taking } \left(\frac{W}{L} \right)_1 = \frac{6}{1}$$

$$\left(\frac{W}{L} \right)_2 = \frac{3}{16}.$$

Differential Amplifier.

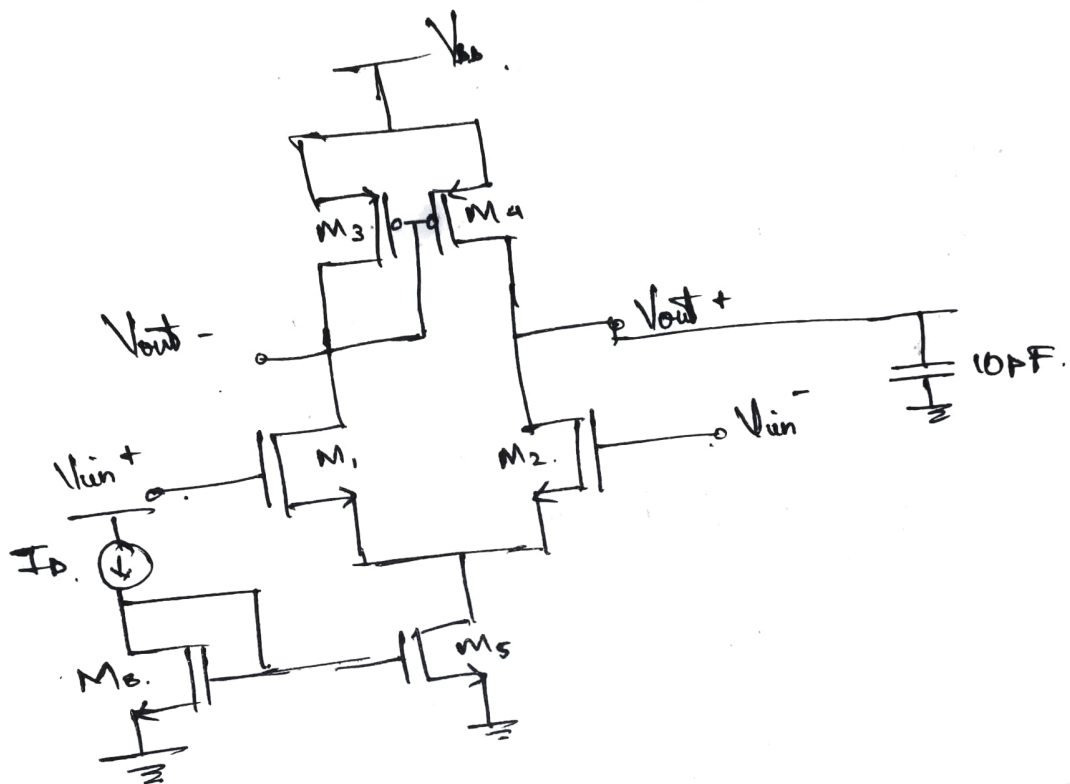

$$C_{in} = 0.045843 \text{ nm}^2 \quad C_{lp} = 0.021201661 \text{ nm}^2$$

$$C_{ox} = 2.484 \times 10^{-3} \text{ F}$$

$$\rightarrow V_{DD} = 5$$

$$G_{BP} = 5$$

$$C_L = 10 \text{ pF}$$

$$I_{CMR+} = 4 \text{ V}$$

$$- \text{---} = \underline{\underline{1.5 \text{ V}}}$$

$$\text{Slew Rate} = \underline{\underline{5 \text{ V}/\mu\text{s}}}$$

$$\textcircled{1} \quad Q = CV \quad \frac{dV}{dt} \times C = \frac{dQ}{dt}$$

$$I_0 = C_L \times \text{Slew Rate}$$

$$= 10 \times 10^{-12} \times 5 \times 10^6 = 50 \times 10^{-6} \text{ A} = \underline{\underline{50 \mu\text{A}}}$$

② Find V_x (M.).

$$V_{ds} > V_{gs} - V_{th} \quad ; \quad V_d - V_s > V_g - V_s - V_{th}$$

$$V_d > V_g - V_{th}$$

$$V_d = V_x$$

$$V_g = I_{CMR} = \underline{4.}$$

$$V_x > V_g - V_{th}$$

$$V_{th} = \underline{0.7.}$$

$$V_x > 4 - 0.7 = \underline{3.3 V.}$$

$$V_x = \underline{3.3 V.}$$

③ Find $M_3 - M_4$ Ratios.

$$V_{TP} = 0.9214 V.$$

$$V_{ds3} = V_{dd} - V_x = 5 - 3.3 V = \underline{1.7 V.}$$

$$V_{ds3} = \underline{1.7 V.}$$

$$I_3 = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L} \right)_3 (V_{gs} - V_{th})^2$$

$$\left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4 = \frac{2 I_3}{\mu_p C_{ox} (V_s - V_g - V_{TP})^2}$$

$$= \frac{2 \times 25 \times 10^{-6}}{\mu_p C_{ox} (5 - 3.3 - 0.9214)^2} = \underline{1.86} = \left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4$$

④ Find $M_1 - M_2$ Ratios.

$$GBP = DC^* P_1 = \frac{g_{m1}}{2 \pi C_L} = 5 \times 10^6$$

$$g_{m1} = 5 \times 10^6 \times 2 \times \pi \times 10 \times 10^{-12} = \underline{314 \text{ ell}}$$

$$g_{m1} = \sqrt{2 I_D \mu_n C_{ox} \left(\frac{W}{L} \right)_1}$$

$$\left(\frac{W}{L} \right)_1 = \frac{(g_{m1})^2}{2 I_D \mu_n C_{ox}} = 17.35 = \underline{\underline{18}}$$

5) Finding M_5 & M_6 .

$$V_{in+} > V_{gs1} + V_{ds5}.$$

$$V_{in+} = I_{CMR-}$$

& V_{gs1} can be obtained from

$$I_D = \frac{C_{ox} \mu_n}{2} \left(\frac{W}{L} \right)_1 (V_{gs1} - V_{th})^2.$$

$$V_{gs1} = \left(\frac{2 I_D}{C_{ox} \mu_n (W/L)_1} \right)^{1/2} + V_{th}.$$

$$V_{gs1} = \left[\frac{2 \times 25 \times 10^{-6}}{C_{ox} \mu_n (18)} \right]^{1/2} + 0.7 = \underline{\underline{0.85V.}}$$

$$\text{Now, } 1.5 > V_{gs1} + V_{ds5}.$$

$$V_{ds5} < 1.5 - V_{gs1} = 1.5 - 0.85.$$


$$V_{ds5} = \underline{\underline{0.64V.}}$$

$$I_{D5} = \frac{C_{ox} \mu_n}{2} \left(\frac{W}{L} \right)_5 (V_{gs} - V_{th})^2.$$

$$\left(\frac{W}{L} \right)_5 = \frac{2 I_{D5}}{C_{ox} \mu_n (V_{ds5})^2} = \underline{\underline{2.14 \approx 3.}}$$

Opamp for a gain of $\underline{\underline{35\text{ dB}}}$. (Differential)
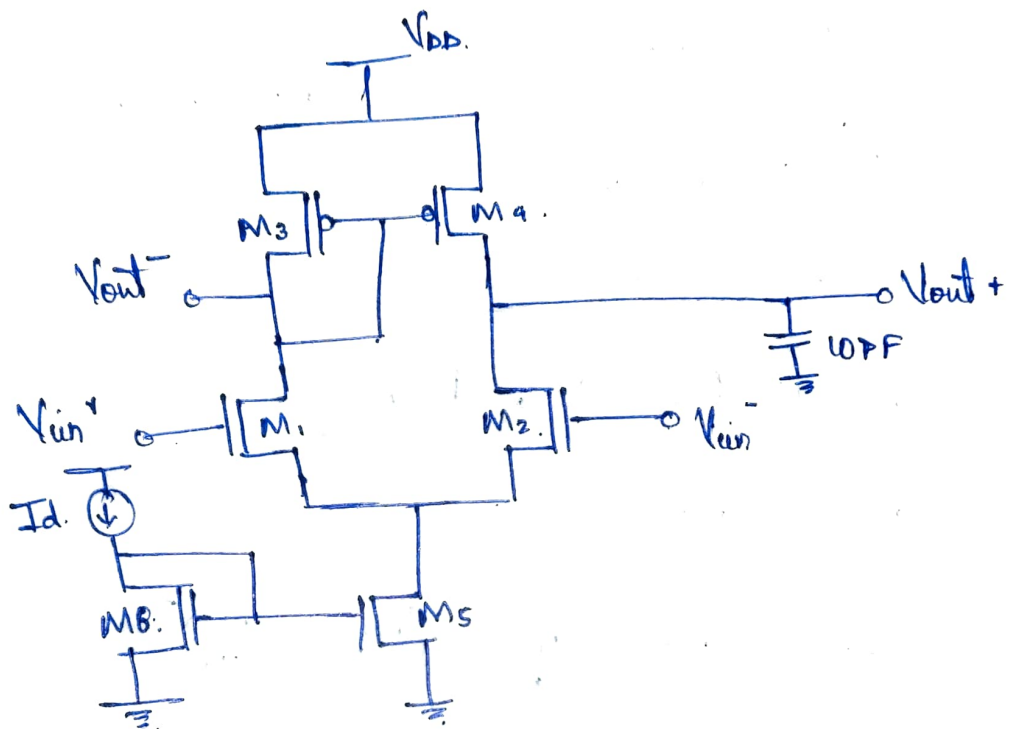
$$A_v = \underline{\underline{35\text{ dB}}} = \underline{\underline{56.23}}$$



Given Parameters:

$$A_v = \underline{\underline{35\text{ dB}}}$$

Selecting

$$GBP \approx \underline{\underline{4\text{ MHz}}}$$

$$cl_n = 0.045843\text{ mm}^2$$

$$cl_p = 0.02120661\text{ mm}^2$$

$$C_{ox} = 2.484 \times 10^{-3}\text{ F}$$

Selecting Parameters:

$$V_{DD} = 5\text{ V}, \quad C_L = 10\text{ pF}$$

$$I_{CMR+} = 4\text{ V}$$

$$I_{CMR-} = 1.5\text{ V}$$

$$V_{tn} = 0.7\text{ V}, \quad V_{dp} = 0.9214\text{ V}$$

$$\text{Slew Rate} = 5\text{ V}/\underline{\underline{\mu\text{s}}}$$

① Finding I_D

$$I_D = C_L \times \text{Slew Rate}$$

$$= 10 \times 10^{-12} \times 5 \times 10^6 = 50 \times 10^{-6} = \underline{\underline{50\text{ }\mu\text{A}}}$$

② Finding V_x at M_1 .

$$V_{ds} > V_{gs} - V_{th} \quad V_d = V_x$$

$$I_{CMR+} = V_g = \underline{\underline{4}} \quad V_d - V_s > V_g - V_s - V_{th}$$

$$V_d > V_g - V_{th}$$

$$V_x > V_g - V_{th}$$

$$V_x = 4 - 0.7 = \underline{\underline{3.3V}}$$

③ Find $M_3 - M_4$ Ratios

$$V_{ds3} = V_{dd} - V_x = 5 - 3.3 = \underline{\underline{1.7V}}$$

$$I_3 = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L} \right)_3 (V_{gs} - V_{thp})^2$$

$$\left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4 = \frac{2 I_3}{\mu_p C_{ox} (V_s - V_g - V_{thp})^2}$$

$$\left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4 = 1.57 \approx \underline{\underline{2}}$$

④ Find $M_1 - M_2$ Ratios:

$$GBP = 4MHz = \frac{g_{m1}}{2\pi C_L} \quad g_{m1} = 4 \times 10^6 \times 2\pi \times 10 \times 10^{-12}$$

$$g_{m1} = 2.514 \times 10^{-4} \text{ S}$$

$$\left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2 = \frac{(g_{m1})^2}{2 I_{D1} \mu_n C_{ox}} = 11.1 \approx \underline{\underline{12}}$$

5) Finding M_s & M_s Ratios.

$$V_{in+} > V_{gs1} + V_{dss}. \quad \text{At } V_{in+} = I_{CMR} -$$

V_{gs1} can be found from

$$I_D = \frac{c \mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_1 (V_{gs1} - V_{tn})^2.$$

$$V_{gs1} = \left[\frac{2 I_D}{c \mu_n C_{ox} \left(\frac{W}{L} \right)_1} \right]^{1/2} + V_{tn}.$$

$$= \left[\frac{2 \times 25 \times 10^{-6}}{c \mu_n C_{ox} (12)} \right]^{1/2} + 0.7 = \underline{\underline{0.89}}.$$

$$1.5 > V_{gs1} + V_{dss}.$$

$$V_{dss} < 1.5 - 0.89 = \underline{\underline{0.61V}}.$$

$$I_D = \frac{c \mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_5 (V_{gs} - V_{tn})^2.$$

$$\left(\frac{W}{L} \right)_5 = \frac{2 I_D}{c \mu_n C_{ox} (V_{dss})^2} = 2.43 \approx \boxed{3}.$$